

Q1: Select the most correct answer: (15 points)

1. What's the equivalent of $t2 = A[A[0]]$ in assembly where the base address of A is in $s0$:

☒ a. lw $t0, 0(s0)$
lw $t2, 0(t0)$

b. lw $t0, 0(s0)$
sll $t1, t0, 2$
add $t1, s0, t1$
lw $t2, 0(t1)$

c. lw $t0, 0(s0)$
add $t1, s0, t0$
lw $t2, 0(t1)$

d. lw $t2, 0(s0)$

24.5
30

2. Which of the following instructions uses PC-relative addressing?

a. addi $t1, t2, 10$
c. jr ra

b. lw $t0, 4(s0)$
d. beq $t0, t1, LABEL$

3. Assume a new instruction **move $t0, t1$** that copies the contents of $t1$ to $t0$. Which of the following standard MIPS instructions is **NOT** equivalent to this operation?

☒ a. add $t0, t1, zero$
☒ c. sub $t0, t1, zero$

b. addi $t0, t1, 0$
☒ d. sub $t0, zero, t1$

0000 0001
0001
0000

4. Decode the machine instruction **0x014B4820**:

☒ a. add $t1, t2, t3$
c. and $t1, t2, t2$

b. addi $t1, t2, 20$
d. sub $t1, t2, t3$

0000 0010 0000 0000
0001 0100

5. Which of the following registers is used with one of J-type instructions?

a. $t0$
☒ b. ra

c. $s0$
d. $s3$

0000 0001
1/20

6. What's the final value stored in $t0$ after executing **lui $t0, 0x1234$** , assuming $t0$ originally contains 0?

☒ a. 0x12340000
c. 0xFFFF1234

☒ b. 0x00001234
☒ d. 0x1234FFFF

7. If a **beq $t0, t1, Label$** at address 0x00400020 branches to 0x00400028, what is the value of **Label**?

☒ a. 1

b. 6

c. 4

d. 8

Student name: _____

Student ID: _____

8. In which case can signed overflow occur in the operation $A - B$:

- a. A is positive and B is positive
- b. $A = 0$ and $B = 0$
- c. A is positive and B is negative
- d. A is negative and B is negative

9. Assume a 4-bits multiplicand and a 4-bits multiplier, what's the size of the ALU that could perform the first-version multiplication :

- a. 8-bits ALU
- b. 16-bits ALU
- c. 4-bits ALU
- d. 32-bits ALU

10. What is the IEEE 754 single-precision representation of the decimal value -1.5 ?

- a. ^{sign} 1011 1111 0110 0000 0000 0000 0000 0000
- ~~b. 0100 0000 0100 0000 0000 0000 0000 0000~~
- ~~c. 1000 0000 0110 0000 0000 0000 0000 0000~~
- d. 1011 1111 1100 0000 0000 0000 0000 0000

↓
01.1

127

S 110...01

Write your choice in the following Answers table. Other answers located outside the table will not be considered.


1.	2.	3.	4.	5.	6.*	7.*	8.	9.	10.
A	C	D	a	B	A	A	C	A	D

12

Student name:

Student ID:

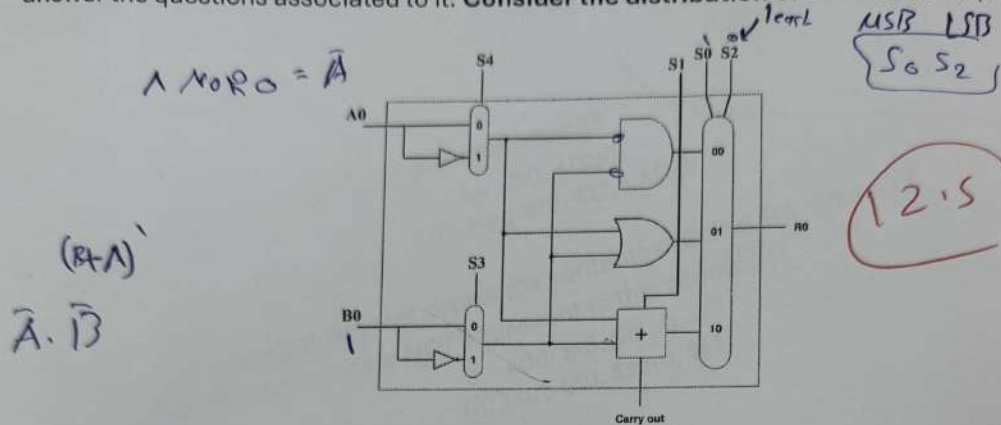Q2: Based on Chapter 3 (ALU Design). Your goal is to understand the following design and answer the questions associated to it. **Consider the distribution of the selectors** (15 points)



1. [2.5 points] Write down input signals to perform subtraction ($A - B$):

S4	S3	S2	S1	S0
0	1	0	1	1

2. [3.5 points] Write down input signals to support a new instruction called "INC A" which increments A by 1 ($A = A + 1$):

A0	B0	S4	S3	S2	S1	S0
A0	0	0	0	0	1	1


3. [3.5 points] Write down input signals to support a new instruction called "DEC A" which decrements A by 1 ($A = A - 1$):

A0	B0	S4	S3	S2	S1	S0
A0	0	0	1	1	1	0

4. [3.5 points] Write down input signals to support a new instruction called "INV A" which inverts A. For example, if $A = 0001$, then INV A returns 1000: 1110

A0	B0	S4	S3	S2	S1	S0
0	1	0	1	0	1	0

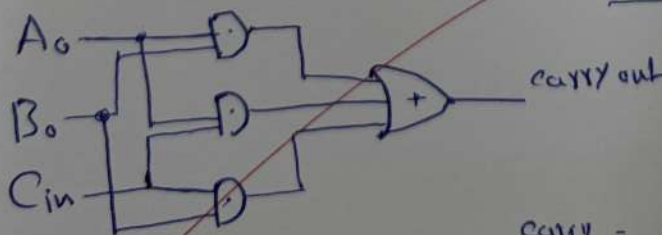5. [2 points] Draw the logic circuit diagram for the carryout in the full adder:



$$\text{carry out} = (A_0 \cdot B_0) + (A_0 \cdot C_{in}) + (B_0 \cdot C_{in})$$